



Mansoura University  
Faculty of Engineering

Electric Circuits  
Course Code: ECE 161  
Fall Semester Exam.




Biomedical Engineering Program  
Level 100

Exam Date: 17-1-2015  
Allowed Time: 2 Hours

**Attempt all questions. Assume any missed data. Full mark is 50**

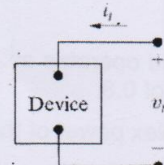
**Q.1.a)** The terminal voltage and terminal current were measured on the device shown and the values of  $v_t$  and  $i_t$  are tabulated.

- Construct a circuit model of the device
- Predict the power this device will deliver to a  $10\Omega$  resistor. [7 Marks]




| $v_t$ (V) | $i_t$ (A) |
|-----------|-----------|
| 100       | 0         |
| 180       | 4         |
| 260       | 8         |
| 340       | 12        |
| 420       | 16        |

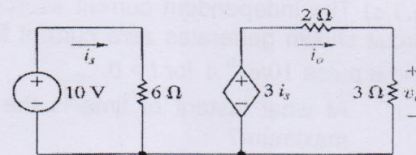
**Q.1.b)** Use Kirchhoff's laws and Ohm's law to find the voltage  $v_o$  as shown in figure. Show that your solution is consistent with the constraint that the total power developed in the circuit equals the total power dissipated. [7 Marks]



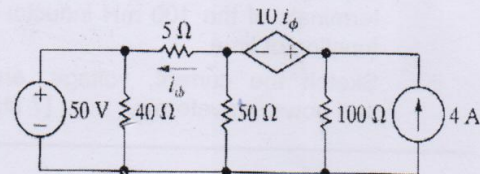**Q.1.c)** Find the current  $i_\phi$  in the circuit shown. Find the power dissipated in the  $100\Omega$  resistor. Find the power developed by the 4A current source. [7 Marks]



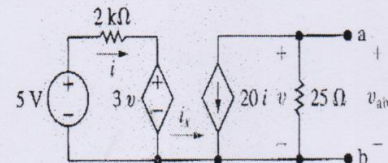
**Q.2.a)** If a  $8K\Omega$  resistor is connected between terminals a & b, use Thevenin equivalent to find the power dissipated in this resistor. [7 Marks]



**Q.2.b)** The switch in the circuit shown has been closed for a long time before it is opened at  $t=0$ . Find


- $i_L(t)$  for  $t \geq 0$
- $i_o(t)$  for  $t \geq 0$
- $v_o(t)$  for  $t \geq 0$

[7 Marks]

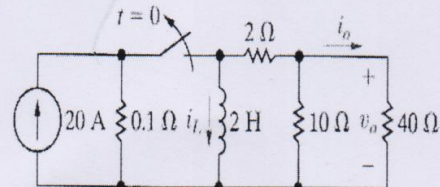


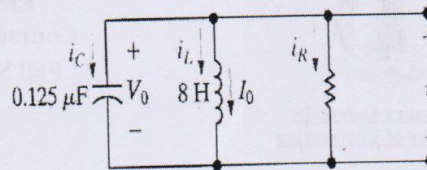**Q.2.c)** For the circuit shown,  $V_o = 0$ ,  
 $I_o = -12.25 \text{ mA}$ .

- Find the value of  $R$  that results in a critically damped voltage response.
- Calculate  $v(t)$  for  $t \geq 0$
- Plot  $v(t)$  versus  $t$  for  $0 \leq t \leq 7 \text{ ms}$  [7 Marks]



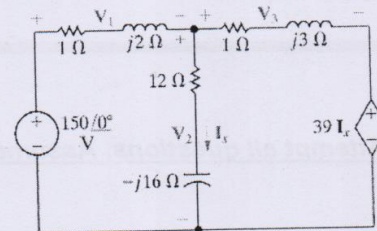**Q.3.a)** Use mesh current method to find the values of  $V_1$ ,  $V_2$ , and  $V_3$  in the circuit shown in figure. [7 Marks]




**Q.3.b)** An electrical load operates at 240V rms. The load absorbs an average power of 8KW at a lagging power factor of 0.8.

- Calculate the complex power of the load.
- Calculate the impedance of the load.

[7 Marks]

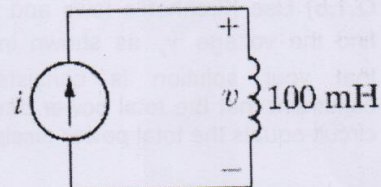**Q.3.c)** The independent current source in the circuit shown generates zero current for  $t < 0$  and a pulse  $10te^{-5t} \text{ A}$  for  $t > 0$ .

- At what instant of time is the current maximum?
- Express the voltage across the terminals of the 100 mH inductor as a function of time.
- Sketch the current, voltage, energy, and power waveforms. [7 Marks]



*My best wishes to all of you!*

*Assis. Prof. Hossam Ft. Din Moustafa*