



Final Exam 2015-2016 – Second Semester


Notes:

- 1- There are additional 5 degrees distributed among all questions.
- 2- Answer **only** five questions from the following six questions.
- 3- Clear Answers may be helpful for both of us
- 4- Time allowed is 120 minutes (24 minutes for each question of the required 5 questions)


1- With aid of characteristic curves, symbols, equations, and Models; briefly describe each of the following with one application for each: JFET, Depletion MOSFET, Enhanced MOSFET, BJT, Zener diode, Shockley diode, and Varactor [11 degrees]

2- For the Circuit Shown in Figure (1); (a) For the DC-analysis : find I_B , I_C , I_E , V_C , V_E , V_{CE} , and discuss the thermal stability (b) for the AC analysis; using Simplified h-model : find the voltage gain , current gain , input impedance , output impedance , and obtain if there is a phase shift between input and output. [11 degrees]

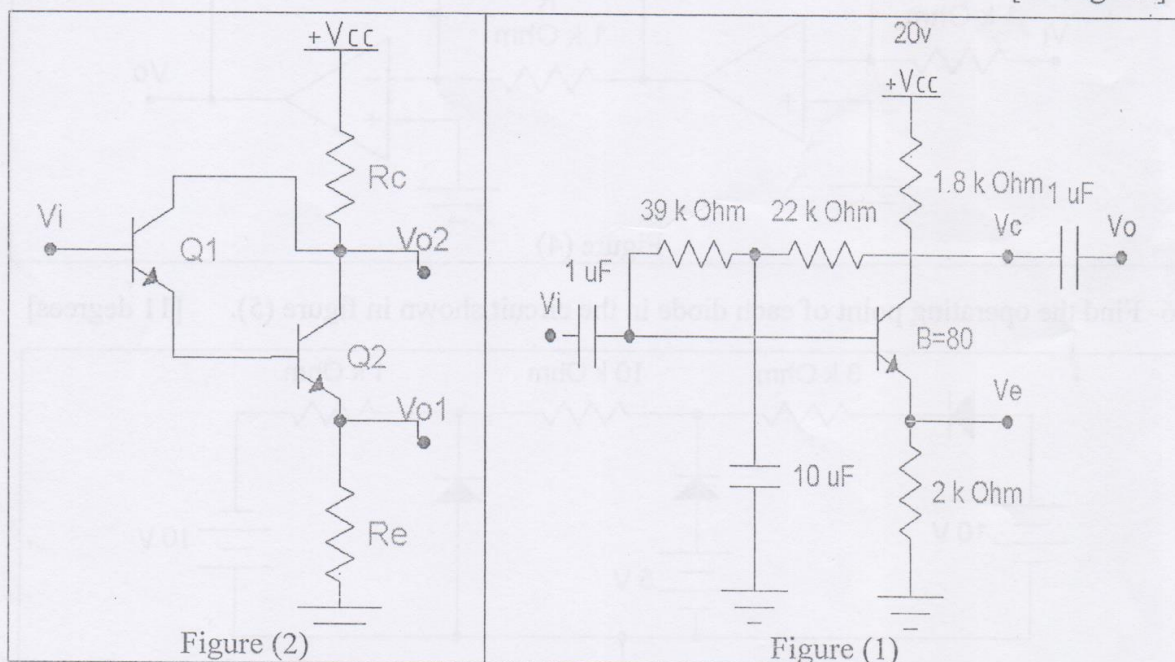
3- For the Darlington Pair circuit shown in Figure (2); find the voltage gain, current gain, input impedance, output impedance, and obtain if there is a phase shift between input and output. [11 degrees]



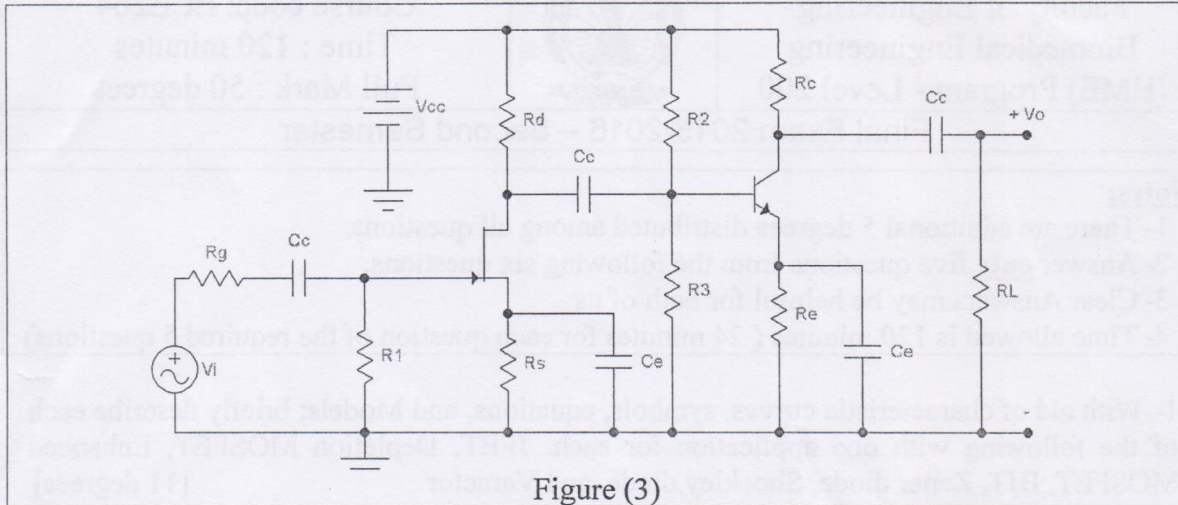
4- For the Circuit shown in figure (3); Find: Voltage Gain (A_v), Current Gain (A_i), Input Impedance (Z_i), Output Impedance (Z_o), and obtain if there is a phase shift between input and output. $h_{ie}=1$, $h_{fe}=30$, $r_d=10k\Omega$, and $\mu=20$ [11 degrees]



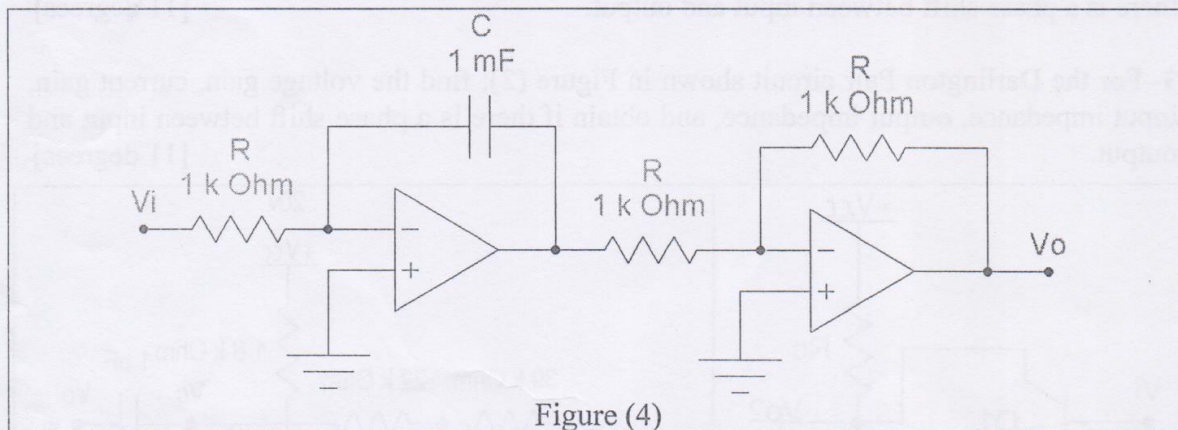5- For the Operational Amplifier circuit shown in Figure(4); (a) Find the mathematical expression which describe the relation between V_o and V_i (b) Describe the operation of this circuit (c) State the main characteristics of the Operational Amplifiers [11 degrees]



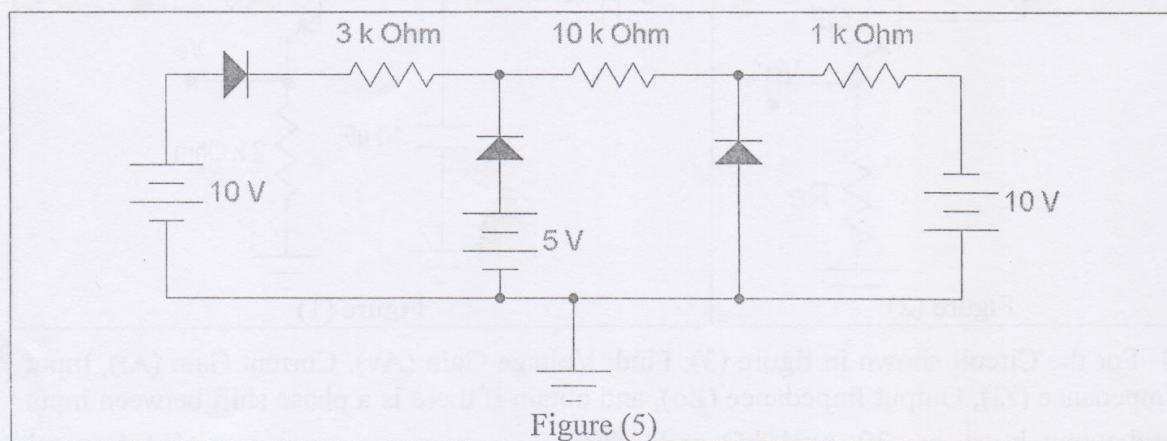6- Find the operating point of each diode in the circuit shown in figure (5). [11 degrees]



Answer the following questions; assuming any missing data.

- 1) a- Compare in a table between the common emitter, common base, and common collector BJT amplifiers.
b- Investigate the effect of connecting a resistance to the emitter terminal in a CE BJT amplifier.
c- Compare between the small signal, and power amplifiers.

(10 Degrees)

- 2) For the common base (CB) amplifier shown in Fig. 1, find the input impedance, voltage gain, overall voltage gain, current gain, short circuit current gain, and output impedance. With $R_C = 10 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$, $V_{CC} = 10 \text{ V}$, and $R_S = 100 \Omega$, what is the value of I so that the input impedance at E is equal to that of the source (i.e. 100Ω) assume $\beta = 100$.

(10 Degrees)

- 3) Use the circuit of Fig. 2 to design a common gate amplifier. Find R_{in} , R_{out} , A_{vo} , A_v , G_v , and G_i for $R_L = 15 \text{ k}\Omega$ and $R_{sig} = 50 \Omega$. What will the overall voltage gain become for $R_{sig} = 50 \Omega$? $10 \text{ k}\Omega$? $100 \text{ k}\Omega$?

(15 Degrees)

- 4) The circuit shown in Fig. 3 consists of two stages:

Stage 1: CE amplifier with $V_{cc} = 12 \text{ V}$, $R_c = 1.0 \text{ k}\Omega$ and $r_e = 5\Omega$.

Stage 2: Darlington emitter follower amplifier with voltage divider bias, given $R_1 = 10 \text{ k}\Omega$, $R_2 = 22 \text{ k}\Omega$, $R_E = 22 \Omega$, $R_L = 8 \Omega$, $V_{cc} = 12 \text{ V}$ and $\beta_1 = \beta_2 = 100$.

(15 Degrees)

- a) Determine the voltage gain of the common-emitter amplifier.
- b) Determine the voltage gain of the Darlington emitter-follower.
- c) Determine the overall voltage gain.
- d) If the circuit is without the Darlington pair, find the gain and compare with that obtained in C.

Answer the following questions; assuming any missing data.

- 1) a- Compare in a table between the common emitter, common base, and common collector BJT amplifiers.
b- Investigate the effect of connecting a resistance to the emitter terminal in a CE BJT amplifier.
c- Compare between the small signal, and power amplifiers.

(10 Degrees)

- 2) For the common base (CB) amplifier shown in Fig. 1, find the input impedance, voltage gain, overall voltage gain, current gain, short circuit current gain, and output impedance. With $R_C = 10 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$, $V_{CC} = 10 \text{ V}$, and $R_S = 100 \Omega$, what is the value of I so that the input impedance at E is equal to that of the source (i.e. 100Ω) assume $\beta = 100$.

(10 Degrees)

- 3) Use the circuit of Fig. 2 to design a common gate amplifier. Find R_{in} , R_{out} , A_{vo} , A_v , G_v , and G_i for $R_L = 15 \text{ k}\Omega$ and $R_{sig} = 50 \Omega$. What will the overall voltage gain become for $R_{sig} = 50 \Omega$? $10 \text{ k}\Omega$? $100 \text{ k}\Omega$?

(15 Degrees)

- 4) The circuit shown in Fig. 3 consists of two stages:

Stage 1: CE amplifier with $V_{cc} = 12 \text{ V}$, $R_c = 1.0 \text{ k}\Omega$ and $r_e = 5\Omega$.

Stage 2: Darlington emitter follower amplifier with voltage divider bias, given $R_1 = 10 \text{ k}\Omega$, $R_2 = 22 \text{ k}\Omega$, $R_E = 22 \Omega$, $R_L = 8 \Omega$, $V_{cc} = 12 \text{ V}$ and $\beta_1 = \beta_2 = 100$.

(15 Degrees)

- a) Determine the voltage gain of the common-emitter amplifier.
- b) Determine the voltage gain of the Darlington emitter-follower.
- c) Determine the overall voltage gain.
- d) If the circuit is without the Darlington pair, find the gain and compare with that obtained in C.