




**Electronics 1**  
**Course Code: ECE 261**  
**Fall Semester Exam.**



**BME Program - Level 200**  
**Exam Date: 11-11- 2019**  
**Allowed Time: 1 Hour**


**Attempt five questions only. Assume any missed data. Full mark is 20.**

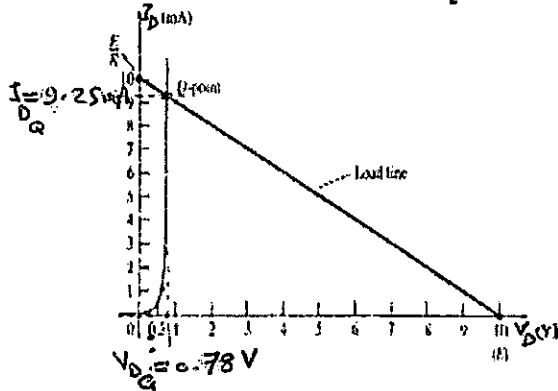**Q.1) Design a diode circuit that satisfies the characteristics shown. [4 Marks]**




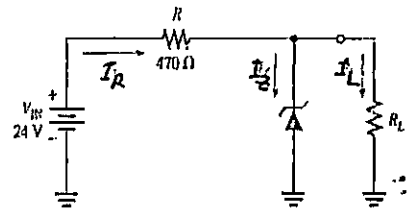**Q.2) Determine the minimum and the maximum load currents and the minimum value of  $R_L$  for which the zener maintains voltage regulation. [4 Marks]**


$$V_z = 12V \quad I_{zmin} = 1mA \quad P_{zmax} = 600mW$$




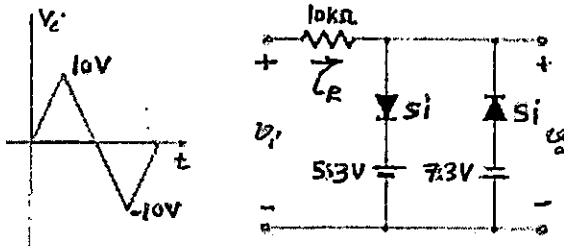
**Q.3) Sketch  $V_o$  and  $i_R$  for the configuration shown below. [4 Marks]**



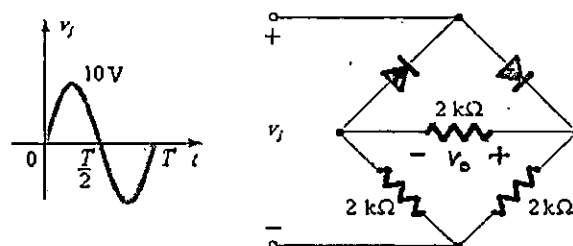**Q.4) Find and sketch  $V_o$ . Determine the DC value. Find the PIV. [4 Marks]**



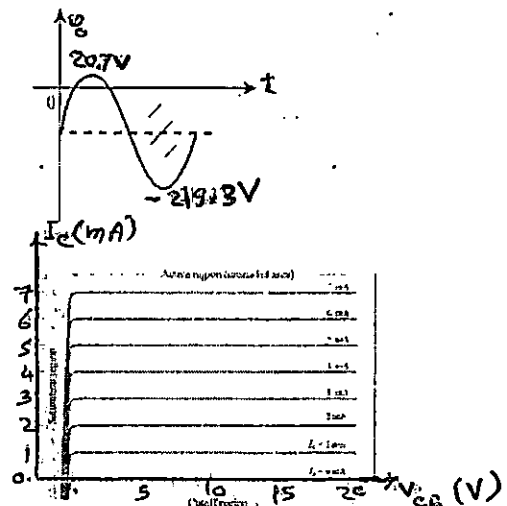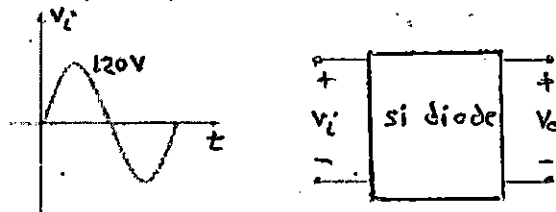**Q5) Design a clamper to perform the function indicated in the figure. [4 Marks]**



**Q.6) Using the characteristics shown:**

- Determine the type of configuration. Define  $\alpha$
- Determine the resulting collector current, if  $I_E = 3mA$  and  $V_{CB} = 10V$
- Determine  $V_{BE}$  if  $I_C = 4mA$  and  $V_{CB} = 20V$

☺My best wishes to all of you☺

Assoc. Prof. Hossam El-Din Moustafa